

**P 4.5-7** Determine  $v_x$  for the circuit shown in Figure P 4.5-7.

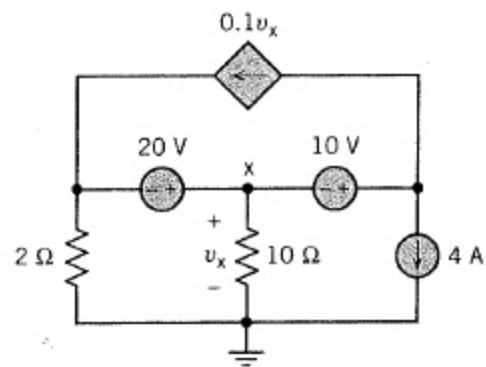


Figure P 4.5-7