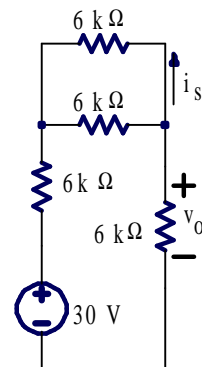



- 21.) Combine some resistors in series and/or parallel to find a single-loop circuit that is equivalent to the given circuit below with respect to finding  $v_o$ . Use the knowledge of  $v_o$  to find the currents through some of the resistors in the given circuit and ultimately, find  $i_s$ . (4/4 points)




- 22.) An ohmmeter is an instrument for measuring electrical resistance directly in ohms. It has two probes. When each probe is attached to a different node in a circuit containing only resistors, the ohmmeter reads the resistance found between the two probes. In the circuit shown below what will an ohmmeter read if it is connected. . . (4/4 points)

a.) . . .to nodes X and Y and

b) . . .to nodes Z and Y?

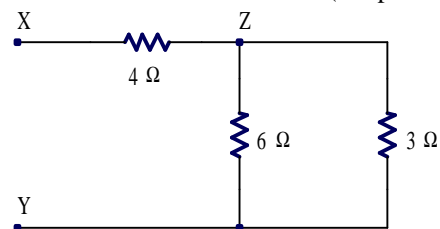

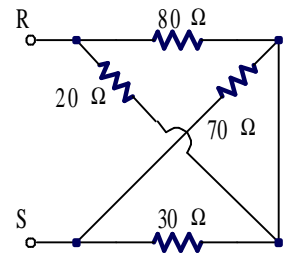23.) What will an ohmmeter read if it is connected to nodes R and S?



24.) Write KVL equations for each circuit shown below. Use Ohm's law to express the KVL equations in terms of two unknowns, the loop current and  $v_8$ . Simplify the equations. By observing the simplified equations assign values to  $V$  and  $R$  in the circuit on the right below so that it is equivalent to the circuit on the left with respect to the voltage across and the current through the  $8\ \Omega$  resistor. (The two simplified KVL equations should then be similar.) Then use the voltage divider equation to find  $v_8$ . Hint: This problem is easier if you label the loop current so that the passive sign convention is satisfied in both circuits for the  $8\ \Omega$  resistor.

