

P 4.5-7 Determine v_x for the circuit shown in Figure P 4.5-7.

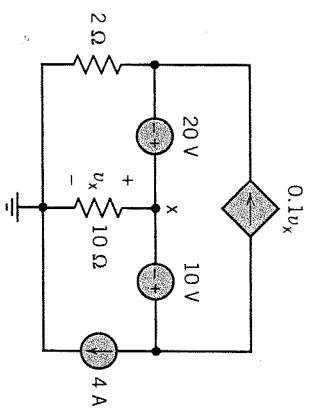


Figure P 4.5-7